

DO NOT WRITE ON IT

Name	Date	Class
------	------	-------

Directed Reading for Content Mastery

Section 2 ■ Electric Current

Section 3 ■ Electrical Energy

Directions: For each of the following write the letter of the term that best completes each statement.

1. A power rating lists the _____ required to operate an appliance.
a. voltage b. watts
2. A closed path through which electrons can flow is _____.
a. voltage b. a circuit
3. A fuse will melt if the _____ in a circuit becomes too high.
a. current b. resistance
4. Current is almost always the flow of _____.
a. electrons b. protons
5. A current has two or more branches in a _____.
a. series circuit b. parallel circuit
6. A car battery is an example of a _____.
a. wet cell b. dry cell
7. The tendency for a material to oppose the flow of electrons is called _____.
a. voltage b. resistance
8. Current has only one loop to flow through in a _____.
a. parallel circuit b. series circuit
9. Current is measured in _____.
a. volts b. amperes
10. Electrical energy is equal to _____ \times time.
a. power b. voltage
11. Electrical power is equal to _____ \times voltage difference.
a. current b. ohms
12. Ohm's law states that the current equals _____ divided by the resistance.
a. amperes b. voltage difference
13. A dry cell is used in a flashlight to convert _____ to light.
a. electrical energy b. static electricity
14. Thin wires have a _____ resistance to electron flow than do thicker wires.
a. greater b. lesser
15. One thousand watts of power used in 60 minutes is _____.
a. 16.7 amperes b. 1 kilowatt-hour

Name	Date	Class
------	------	-------

SECTION

Reinforcement

Electric Current

Directions: Circle the term in parentheses that makes each statement true.



1. A negatively charged object has (more, fewer) electrons than an object that is neutral.
2. Electrons flow from areas of (higher, lower) voltage to areas of (higher, lower) voltage.
3. Voltage difference is measured in (amperes, volts).
4. Electrons passing through a lamp (gain, lose) some voltage as they light the lamp.
5. Voltage (varies, is the same) in all parts of a series circuit.
6. The current in a circuit is measured in (volts, amperes).
7. Current is almost always the flow of (electrons, protons)
8. When a dry cell is connected in a series, the flow of electrons moves from the (positive, negative) terminal to the (positive, negative) terminal.
9. In a dry cell, the carbon rod releases electrons and becomes the (positive, negative) terminal.
10. The voltage difference between the two holes in a wall socket is (12 volts, 120 volts).
11. A car battery is an example of a (dry, wet) cell.
12. Resistance is measured in (ohms, volts).
13. Copper has a (higher, lower) resistance to electron flow than tungsten.
14. According to Ohm's law, ($I = V/R$, $V = IR$)
15. The symbol for ohm is (Ω , °).
16. In the equation $I = V/R$, I is expressed in (ohms, amperes).
17. In the equation $I = V/R$, V is expressed in (volts, ohms).
18. The (+, -) terminal of a dry cell identifies the location of the carbon rod.
19. A wire with a resistance of 3Ω has a (greater, lesser) resistance to electron flow than a wire with a resistance of 5Ω .
20. If two copper wires are the same length, but different thicknesses, the (thinner, thicker) wire has greater resistance.

Name _____ Date _____ Class _____

Directed Reading for
Content Mastery
Electricity
Directions: Complete the sentences by circling the correct words.

Electricity is **1.** (static, parallel) when electric **2.** (charges, circuits) accumulate on an object by gaining or losing **3.** (branches, electrons) that move more easily in **a(n) 4.** (conductor, insulator) than they do in a(n) **5.** (conductor, insulator).

Electricity in the form of a **6.** (current, series) flows from object to object from **7.** (low, high) voltage to **8.** (low, high) voltage. This voltage **9.** (parallel, difference) can be produced by a **10.** (battery, generator) or by a **11.** (battery, generator) at a power plant. Electrical **12.** (charges, circuits) can be **13.** (series, branches) with one loop, current to flow through or they can be **15.** (static, parallel) with two or more **16.** (series, branches) for the electricity.

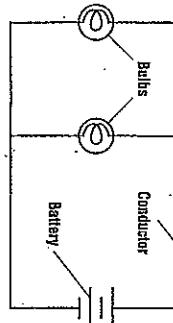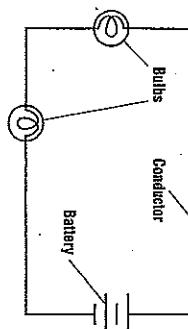Directions: Use the following diagrams to answer the questions below.

17. This is a _____ circuit. 18. This is a _____ circuit.

19. In which circuit will the brightness of the bulbs be diminished as more bulbs are added? _____

20. In which circuit will both lights go out if one light is turned off?

21. Which circuit is used to provide electricity to houses?

Name _____ Date _____ Class _____

SECTION
3
Reinforcement
Electrical Energy
Directions: Use the terms and statements below to complete the table.

rate at which electrical energy is converted to another form of energy

The current has only one loop to flow through.

kilowatt

watt

The current has more than one branch.

parallel circuit

series circuit

insulation to melt

fuses

circuit breakers

a fire

Power = current \times voltage difference $P = I \times V$ **Important Facts About Electric Circuits**

1. There are two types of electric circuits.

Two types of circuits:

a.

b.

Definitions of these circuits:

c.

d.

2. A household circuit can contain many appliances.

Too many appliances can cause:

a.

b.

For protection, household circuits contain:

c.

d.

3. The electrical power of a circuit can be measured.

Definition of electrical power:

a.

b. Name:

c. Abbreviation:

d. Term for 1,000 units:

e. Abbreviation for 1,000 units:

Determining the electrical power of a circuit:

f. Expression:

g. Formula: